



Figure 5 Comprising six independent windings that offer more than 500 configurations, Coiltronics' VP1-1400 serves as a combination feedback and flyback transformer in this application. Connect the windings as shown.