



Figure 2 A resistive divider brings a 5V signal in range for a 3.3V input.

---