



Figure 3 A 5V CMOS device can directly drive TTL inputs.

---