



Figure 1 In this unconventional step-down circuit, capacitors  $C_1$  and  $C_2$  charge in series and discharge in parallel, reducing the voltage applied to regulator  $IC_1$ .