



Figure 1 Use this versatile precision rectifier circuit to recover a signal's positive peaks, negative peaks, or both in full-wave mode.