



Figure 1 This basic circuit combines a current-output DAC, IC₁, with a single-ended-to-differential op-amp stage—IC₂, IC_{3A}, and IC_{3B}—to generate the desired outputs.