



Figure 1 This typical quickly responding constant-current sink uses a bipolar transistor but suffers from base-current-induced error. Its nominal output current is $I_{OUT} = (V_{REF}/R_1) - I_B$.