



Figure 2 Adding base-current error compensation improves the circuit's performance. Using perfectly matched resistors simplifies the output-current equation to  $I_{OUT} = (V_{REF}/R_1)$ .