



Figure 4 Adding $R_{SPEEDUP}$ improves the performance of a two-transistor Darlington output stage.