



Figure 2 When the voltages across R_1 and C_2 are equal, $V_{C1} = -V_{R2}$, $V_{C1} + V_{R1} = V_{S1}$, and $V_{C2} + V_{R2} = V_{S2}$.