



Figure 2 During the first pulse of the microcontroller's output-pulse sequence, the NAND gate's output clears the shift register and lights all of the display's segments.