



Figure 1 Using a tapped inductor extends a boost-topology switching regulator's practical output-voltage range.