



Figure 1 Connected in cascade, a low-dropout linear regulator and a switched-mode power supply improve output-voltage ripple and maintain overall efficiency. (Note: In IC₁'s part designation, "XX" represents the regulator's output voltage.)