



Figure 2 Measured from the positive-going edge of IC₂'s output to the circuit's output at Q₁'s collector, the relative jitter averages less than 1 μsec.