



Figure 1 A two-wire resistive voltage-divider interface encodes a four-row-by-four-column keypad.