



Figure 2 Using the microcontroller's analog reference-voltage output and ratiometric analog-to-digital conversion ensures correct encoding of the keypad.