



Figure 1 A one-IC amplifier with a voltage gain of three provides flat response to more than 60 MHz.