



Figure 1 One IC and a few passive parts directly display temperature on an external voltmeter. See Table 1 for values for R_1 , R_2 , and R_3 .