



Figure 2 The finished circuit design eliminates inductors and substitutes gyrators as “supercapacitors.” Using medium-tolerance components and quad op amps to reduce component count minimizes circuit cost.