



Figure 2 A gain-of-three high-voltage amplifier derives forcing voltages as high as $\pm 22\text{V}$ from voltages of $\pm 7\text{V}$ from test equipment.