



Figure 3 This floating-regulator circuit produces $\pm 5V$ floating-power-supply voltages V_{CC} and V_{EE} referenced to the test input's forcing voltage.