



CONNECT REFERENCE
GROUND HERE.

Figure 3 Buck regulators have large circulating currents in the input capacitor and the synchronous switch ground. Keep the reference ground away from those nodes.