



Figure 5 This 1.25-MHz buck-regulator circuit finds use in a high-volume consumer product.