



Figure C You can stop ground loops with the transformer (a), the differential amplifier (b), and the ground-loop eliminator (c).

---