



Figure 1 In a conventional ESD-suppression circuit, diodes clamp an amplifier's input voltage to its power-supply rails but introduce unwanted leakage currents.