



**Figure 16**  $C_{OUT}$  dominates the regulator's dynamic response;  $C_{IN}$  is much less critical. Parasitic inductance and resistance limit the capacitor's effectiveness at frequency. The capacitor's value and dielectric significantly influence the load-step response. Excessive trace impedance is also a factor.

---