



Figure 17 A stepped 0.5A load to Figure 16's circuit (Trace A) with $C_{IN}=C_{OUT}=10\ \mu\text{F}$ results in Trace B's regulator output. The use of low-loss capacitors promotes controlled output excursions.
