



Figure 2 A practical regulator-load tester includes a FET driver and Q_1 switch. The oscilloscope monitors the current-probe output and regulator response.