



Figure 4 Figure 2's circuit responds to the FET driver's output (Trace A), switching a 1A load (Trace B) in 15 nsec.

---