



Figure 5 In this conceptual closed-loop-load tester, A_1 controls Q_1 's source voltage, setting the regulator's output current. Q_1 's drain-current waveshape is identical to A_1 's input, allowing linear control of the load current. The voltage and current monitors match those in Figure 1.