



Figure 6 In a detailed closed-loop-load tester, the dc-level and pulse inputs feed A_1 to the Q_1 current-sinking-regulator load. Q_1 's gain allows a small A_1 output swing, permitting wide bandwidth. The damper network, feedback, and peaking trims optimize edge response.