



Figure 8 This circuit matches that of Figure 6 but with a bipolar transistor. Q₁'s reduced input capacitance simplifies loop dynamics, eliminating compensation components and trims. The trade-off is a halving of speed and a base-current-induced 1% error.