



Figure 1 A phase-shift RC-oscillator circuit uses an emitter-coupled amplitude limiter.