



Figure 3 For the component values in Figure 1, the oscillator's output voltage reaches full amplitude in approximately 400  $\mu$ sec, or 15 cycles after start-up.