



Figure 4 A 100W light bulb at a 20-cm distance illuminates the collector-emitter voltage of a phototransistor with a feedback circuit (a) and with no feedback (b). Saturation of the circuit with no feedback prevents signal detection.