



NOTE: IC₁'S PINS WITH —○ INDICATE NO CONNECTION.

Figure 1 An LED, a microprocessor, two resistors, and one capacitor constitute the entire circuit.