



Figure 2 This buffered-output, 18-MHz oscillator features a resonant circuit that doesn't rely on mutual coupling for operation.