



**Figure 2** Connecting one of the microcontroller's outputs, Pin 2, to the LED's cathode applies reverse bias that charges the LED's internal capacitance to the supply voltage. Connecting the LED's cathode to Input Pin 3 attaches a high-impedance load to the LED. (Note that pin numbers are representative only and not actual pin numbers.)