



Figure 2 A two-diode rectifier and lamp-control bidirectional thyristor share a common return path to the ac line.