



Figure 3 An optoisolator separates the bidirectional thyristor's high-current ac-line return path from the microcontroller's power supply.