



Figure 1 Combining a programmable-gain, chopper-stabilized amplifier with an instrumentation amplifier delivers high gain and low noise over a subaudible frequency range.