



Figure 2 A buck regulator steps down the input voltage (a), and you can make a water-wheel equivalent (b).