



Figure 1 Use this third-order, 30-kHz filter circuit to observe a Class D amplifier's output signal on an oscilloscope.