



Figure 1 An analog-voltage-to-pulse-width converter features minimal parts. Subgraphs show timing-network and output-voltage waveforms. IC<sub>1</sub>'s unlabeled pins are available for user functions.