



**Figure 1** In this typical method for drawing power from a USB port, the storage-element current is limited to a fixed value that is less than optimal.