



Figure 1 For efficient operation at output voltages of 3.3V or higher, a charge pump comprising D₂ and C₅ provides a voltage boost that provides sufficient drive for IC₁'s internal switching transistor.