



Figure 2 At outputs as low as 1.8V, efficient operation at low input voltages benefits from an added low-dropout regulator, IC₂, for the Boost pin, which extends the circuit's input-voltage range.