



Figure 3 At a maximum input voltage of 36V (V_{IN}), waveforms at the SW and Boost pins show a 5V boost-voltage margin for the circuit of Figure 2.