



Figure 1 Based on a low-cost microcontroller, this dot/bar LED driver operates in linear or logarithmic modes.