



Figure 2 One method of driving an LED illuminator samples current through a string and adjusts the voltage across the entire string to maintain a constant current.